



National University of Modern Languages
(NUML)

Assignment # 01 Fall 2023

Date: -8-Oct- 2023

Program: Applied Physics Class & Section: BSCS-1

Course Code & Name: _____

Duration till: 12-Oct-2023

Instructor's Name: _____


Total Marks: 4 Marks

Attempt all questions:

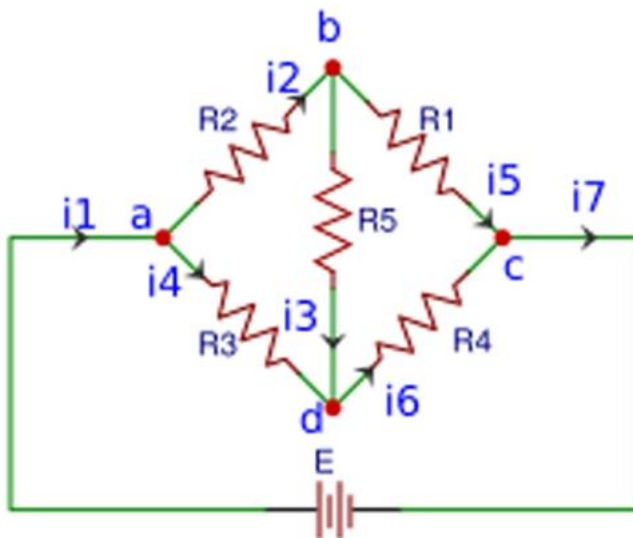Q 1) : Solve the circuit by using KCL

(Mark 4)

a): find the unknown currents in the figure below. Given $i_1 = 10A$, $i_2 = 6A$, $i_5 = 4A$.



***** Good Luck*******