



National University of Modern Languages  
(NUML)

**Assignment # 02 Fall 2023**

**Date:** -23-Oct- 2023

Program: Applied Physics Class & Section: BSCS-1

Course Code & Name: \_\_\_\_\_


Duration till: 27-Oct-2023

Instructor's Name: \_\_\_\_\_


Total Marks: 4 Marks

**Attempt all questions:**

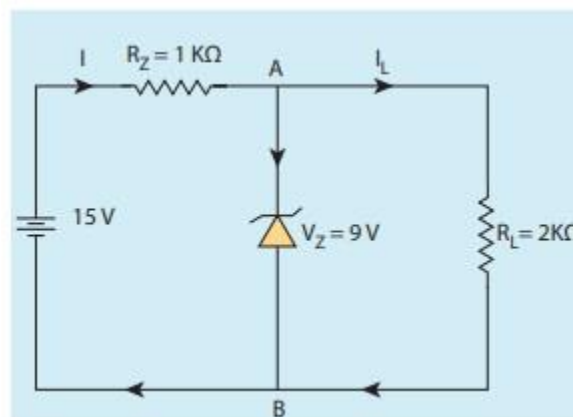
**Q 1 ) :** Find the current through the Zener diode when the load resistance is  $1\text{ K}\Omega$ . Use diode approximation. **(Mark 1)**



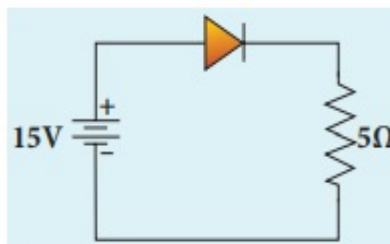
**Q2):** An ideal diode and a  $5\text{ }\Omega$  resistor are connected in series with a  $15\text{ V}$  power supply as shown in figure below. Calculate the current that flows through the diode. **(Mark 1)**



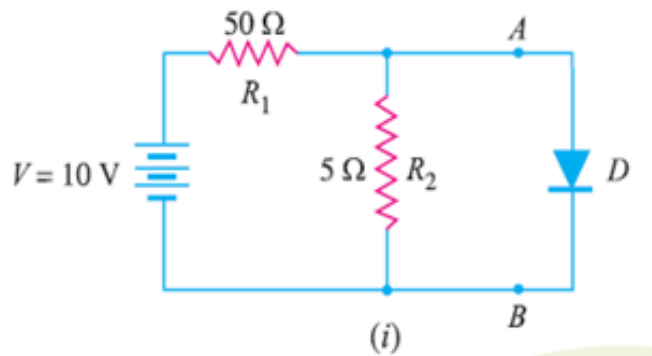**Q3):** Find the current through the diode in the circuit shown in Fig. Assume the diode to be ideal. **(Mark 1)**



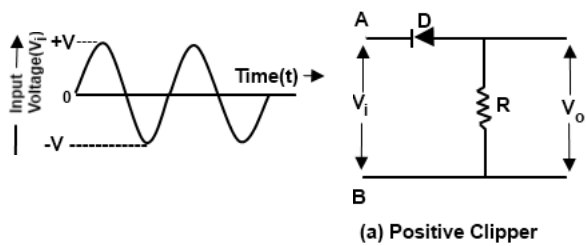**Q4):** Sketch the shape of the output voltage waveform for this "clipper" circuit, assuming an ideal diode with no forward voltage drop: **(Mark 1)**



**\*\*\* Good Luck\*\*\*\*\***