



National University of Modern Languages  
(NUML)

### Assignment#3 Fall 2023

Date: -19-Dec- 2023

Program: Applied Physics

Class & Section: BS-1B

Course Code & Name: \_\_\_\_\_

Duration till: 27-Dec-2023

Instructor's Name: \_\_\_\_\_

Total Marks: 25 Marks

#### Attempt all questions:

Each question carries equal marks(Mark 5).


Q 1 ) : Calculate the  $V_{34}$  and verify the KCL. Calculate  $I_{R1}$ ,  $I_{R2}$ ,  $I_{R3}$ ,  $I_{tot}$  and  $R_{eq}$  as shown in Figure (1)

Q2): Calculate the voltage across each resistor as shown in Figure (2)


Q3) Calculate the output voltage across  $R_2$  as shown in Figure (3) as the diode is Practical and draw a waveform. Calculate the current through  $R_2$

Q4): Calculate the output voltage across  $R_1$  and  $R_2$  as the diode is practical as in Figure(4).

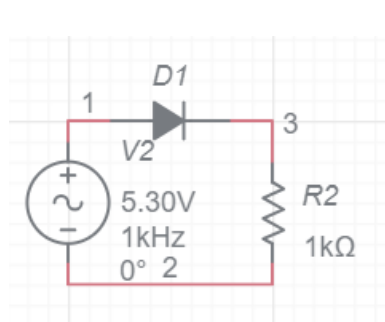
Q5): Covert the current source into a voltage source. Calculate the voltage across  $R_2$  and  $R_1$  in the Figure(5).




Figure(3)

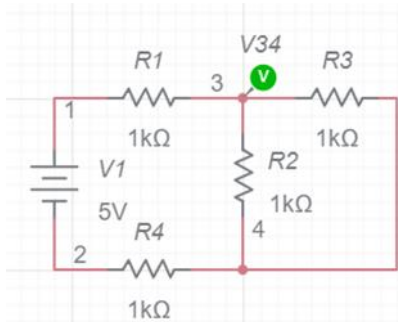


Figure(1)

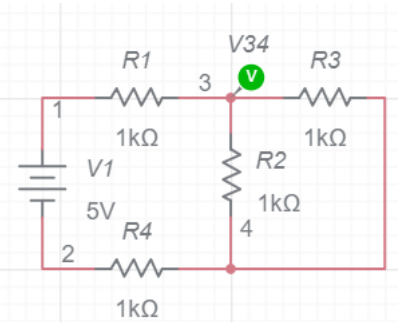

Figure(2)

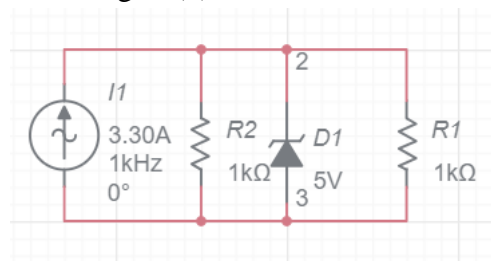

Figure(5)

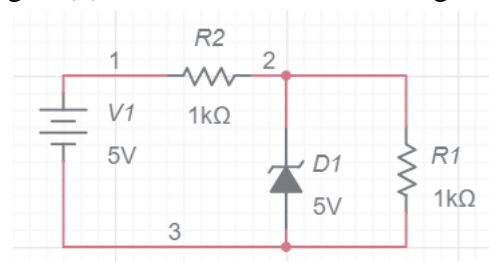

Figure(4)

\*\*\* Good Luck\*\*\*\*\*